

NAME \rightarrow MALAY GHOSH.


REG. NO. \rightarrow 12321607.

ROLL NO. \rightarrow 67.

Malay Ghosh
Reg. no. 12321607
Roll no. 67

Assignment Questions :-

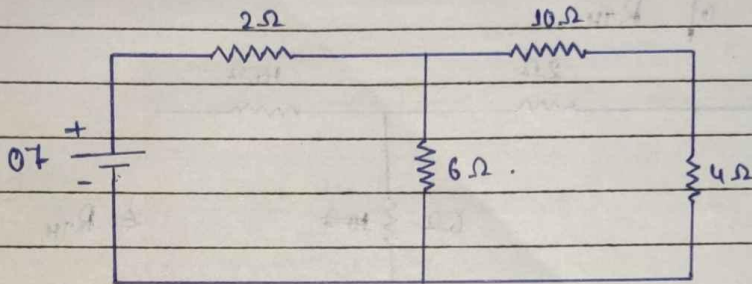Q. 1) Apply the Thevenin and Norton theorem to find the value of current across 4Ω , if the input applied voltage is the last two digits of your registration number.




Soln Using Thevenin's theorem :-

Step 1) Identify the load resistance (R_L).

$$\therefore R_L = 4\Omega.$$

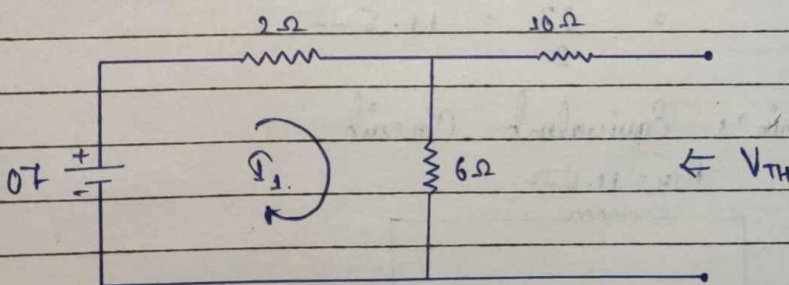Step 2) Remove (R_L) from the above given circuit and calculate I_1 & V_{TH} .



Hence,

Applying KVL in loop 1 -

$$-7 + 2I_1 + 6I_1 = 0$$

$$\Rightarrow -7 = -8I_1$$


$$\Rightarrow I_1 = \frac{7}{8} \text{ A}$$

$$\therefore V_{TH} = I \cdot R$$

$$= \frac{7}{8} \times 6^3$$

$$= \frac{21}{4} = 5.25 \text{ V}$$

Step 3) Calculation of R_{TH}

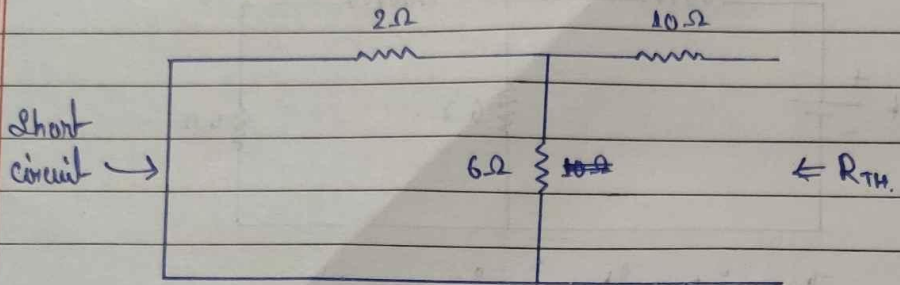

$$\therefore R_{TH} = (2 \parallel 6) + 10$$


$$= \frac{2 \times 6}{2 + 6} + 10$$

$$= \frac{3}{2} + 10$$

$$= \frac{23}{2} = 11.5 \Omega$$

Step 4). Thevenin's Equivalent Circuit.

$$R_{TH} = 11.5 \Omega$$

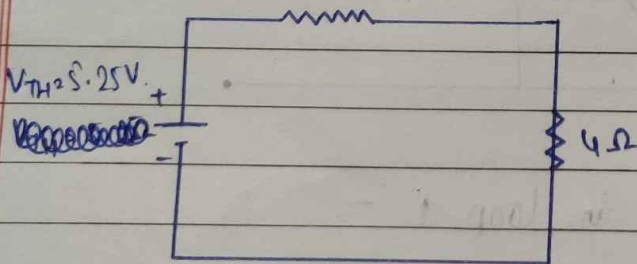


$$\therefore V_{TH} = I \cdot R_{TH}$$

$$\Rightarrow I = \frac{V_{TH}}{R_{TH}} = \frac{5.25}{(11.5 + 4)} = \frac{5.25}{15.5}$$

$$= 0.34 \text{ A}$$


Using Norton's Theorem :-

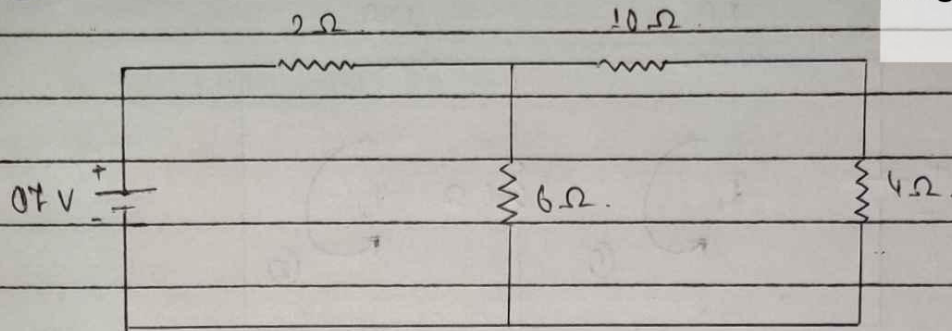Malay Ghosh
Reg. no. 12321607
Roll no. 67



Step 1) Identifying the load resistance (R_L).
 $\therefore R_L = 4\Omega$.

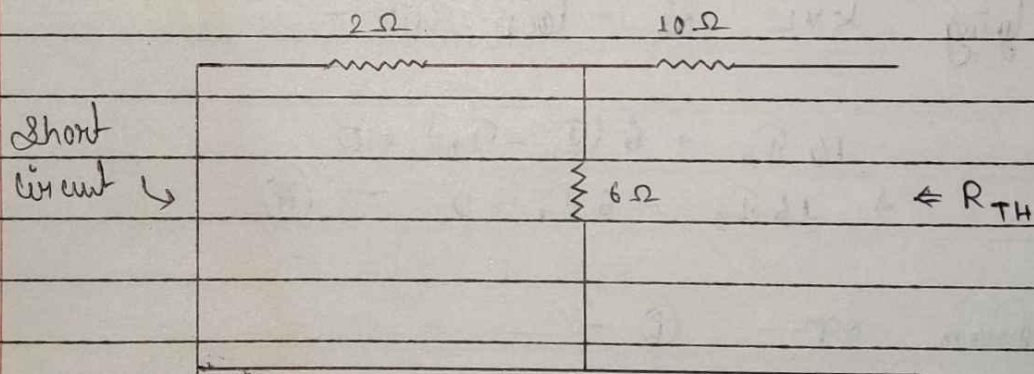Step 2) Temporarily removing the load resistance (R_L) and calculating the value of R_{TH} (Thevenin Equivalent Resistance).



$$\therefore R_{TH} = (2 \parallel 6) + 10.$$

$$= \left(\frac{2 \times 6}{2 + 6} \right) + 10.$$

$$= 3 \frac{12}{8} + 10.$$


$$= \frac{23}{2} = 11.5 \Omega.$$

Step 3) Calculation of I_N (Norton current).

Malay Ghosh

Reg. no. 12321607

Roll no. 67

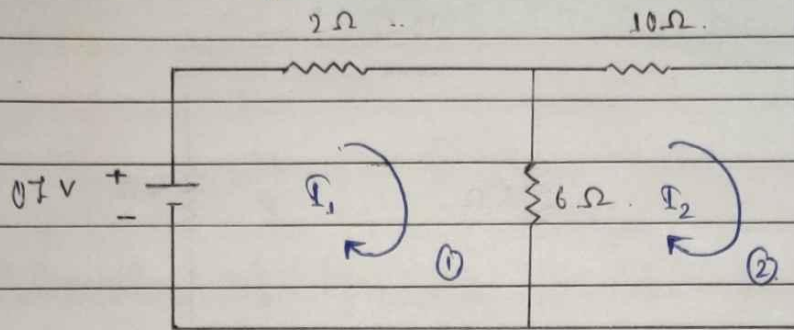

Applying KVL at loop ① —

$$-7 + 2I_1 + 6(I_1 - I_2) = 0$$

$$\Rightarrow -7 + 8I_1 - 6I_2 = 0$$

$$\Rightarrow 8I_1 - 6I_2 = 7 \quad \text{--- (i)}$$

Applying KVL at loop ② —

$$10I_2 + 6(I_2 - I_1) = 0$$

$$\Rightarrow 16I_2 - 6I_1 = 0 \quad \text{--- (ii)}$$

\therefore From eqn (i) —

$$I_1 = \frac{7 + 6I_2}{8}$$

From eqn (ii) —

$$16I_2 - 6\left(\frac{7 + 6I_2}{8}\right) = 0$$

$$\Rightarrow 16I_2 - \frac{3(7 + 6I_2)}{4} = 0$$


$$\Rightarrow 16I_2 - \frac{(21 + 18I_2)}{4} = 0$$

$$\rightarrow \frac{64I_2}{4} - 21 - 18I_2 = 0$$

$$\rightarrow 46I_2 = 21$$

$$\rightarrow I_2 = \frac{21}{46} = 0.45 \text{ A} = I_N$$

Step 4) Norton's equivalent circuit.

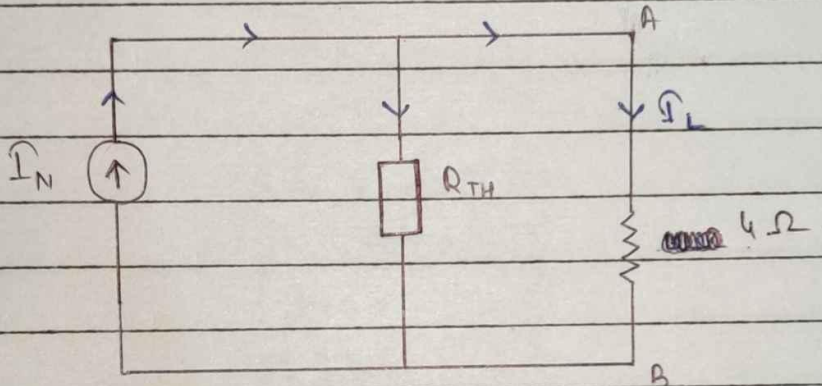

By Current Division Rule,



$$I_L = I_N \times \frac{R_{TH}}{R_{TH} + 4}$$

$$= \frac{0.45 \times 11.5}{11.5 + 4}$$


$$= \frac{5.175}{15.5}$$

$$= 0.33 \text{ A}$$

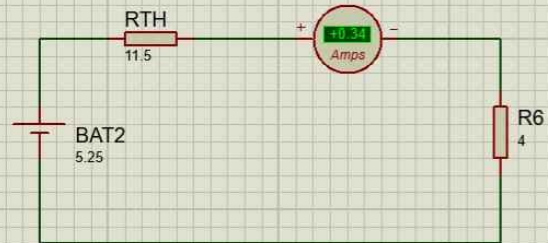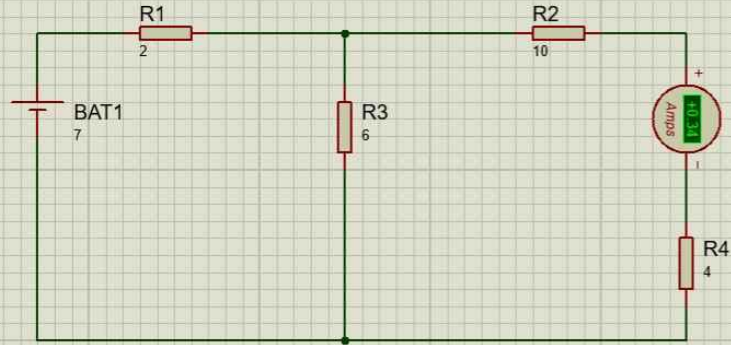NAME:- Malay Ghosh
REG. NO. :- 12321607
ROLL NO. :- 67
SECTION:- K23GD



THEVENIN'S THEOREM

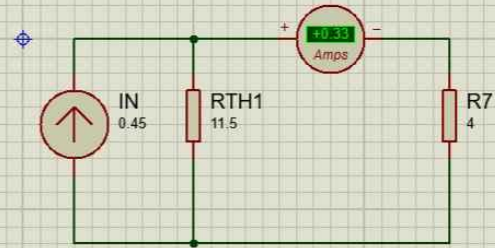

NORTON'S THEOREM

Q. 2. Implementation of a Boolean function using 4:1 multiplexer on proteus software. The Minterms will be implementation of Decimal to Octal conversion of your Registration number.

Sol^m

Registration number = $(12321607)_{10}$.

Into Octal :-


$$\begin{array}{r} 8 \overline{) 12321607} \\ 8 \overline{) 1560200} = 7 \\ 8 \overline{) 192825} = 0 \\ 8 \overline{) 24068} = 1 \\ 8 \overline{) 3008} = 4 \\ 8 \overline{) 376} = 0 \\ 8 \overline{) 47} = 0 \\ 5 = 7. \end{array}$$


\therefore Octal number = $(57004107)_8$.

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$Y(A, B, C) = \Sigma(1, 0, 4, 7)$$

A \ BC	$\overline{A}\overline{B}\overline{C}$ 00	$\overline{A}\overline{B}C$ 01	$\overline{A}B\overline{C}$ 10	$\overline{A}BC$ 11
$(\overline{A}) \rightarrow 0$	0	1	2	3
$(A) \rightarrow 1$	4	5	6	7

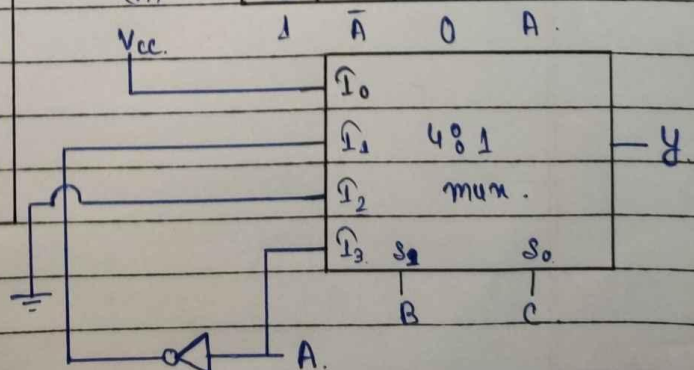

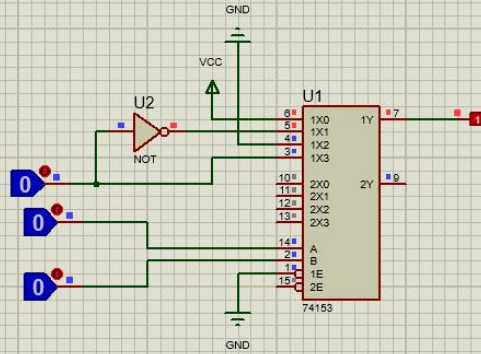

NAME:- Malay Ghosh
 REG. NO. :- 12321607
 ROLL NO. 67
 SECTION:- K23GD

Truth Table

A	B	C	Y(0, 1, 4, 7)
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1



sketch_nov12a

```
const int ProxSensor=7;
const int led = 10;

void setup() {
  pinMode(led, OUTPUT);
  pinMode(ProxSensor, INPUT);
  Serial.begin(9600);
}

void loop() {
  if(digitalRead(ProxSensor)==HIGH)
  {
    digitalWrite(led,HIGH);
    Serial.println("MALAY GHOSH..12321607")
  }
  else
  {
    digitalWrite(led,LOW);
    Serial.println("Roll no. 67");
  }
}
```

Malay Ghosh

Reg. no. 12321607

Roll no. 67



